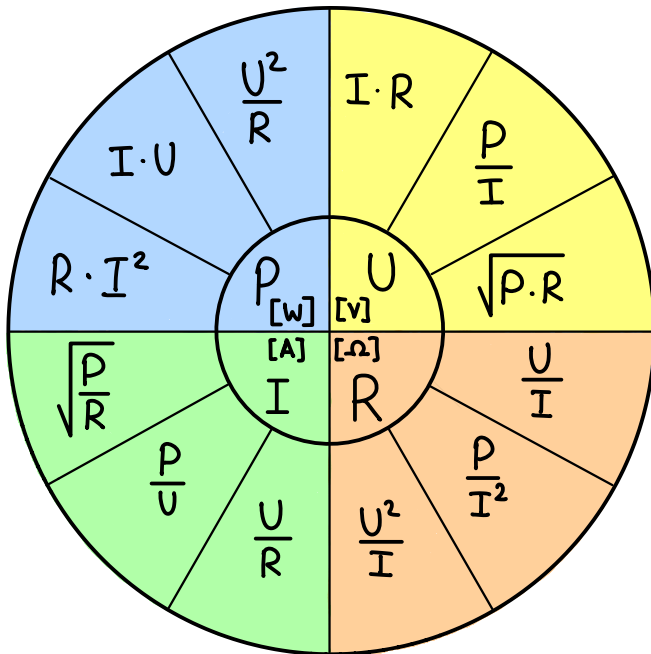


Introduction

Decimal prefixes

T	tera	10^{12}	μ	micro	10^{-6}
G	giga	10^9	n	nano	10^{-9}
M	mega	10^6	p	pico	10^{-12}

ET basis



Current strenght (I)

$$I = \frac{\text{electric charge}}{t} \quad [A]$$

Current density (J)

$$J = \frac{I}{F} \quad [A/mm^2]; \quad F = \text{cross section}$$

In houses, $J = 2 \dots 10 \text{ A/mm}^2$

Resistance

$$R = \frac{U}{I} \quad [\Omega]$$

Kirchhoff's current law (KLC)

$$\sum_{k=1}^n \underline{I}_k = \underline{I}_1 + \underline{I}_2 + \dots + \underline{I}_n = 0$$


Kirchhoff's voltage law (KVC)

$$\sum_{k=1}^n \underline{U}_k = \underline{U}_1 + \underline{U}_2 + \dots + \underline{U}_n = 0$$

Voltage drop/divider formula

$$U_0 = U_1 \frac{R_2}{R_1 + R_2}; \quad U_0 = \frac{R_2 U_1 + R_1 U_2}{R_1 + R_2}$$

Resistance temperature dependance

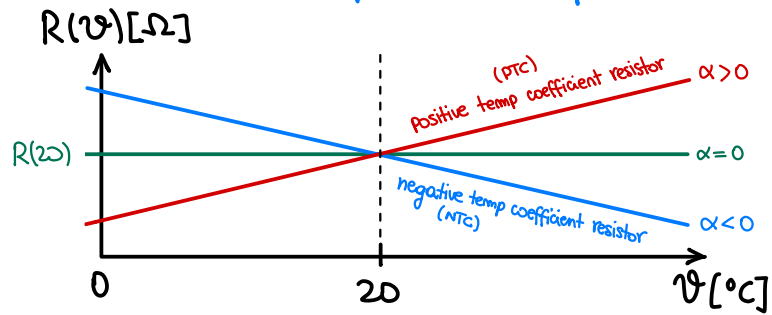

$$R(\theta) = R_{20} (1 + \alpha (\theta - 20^\circ)) = R_{20} (1 + \alpha \cdot \Delta T)$$

$$\alpha = \left[\frac{1}{K} \right] \rightarrow \alpha_{\text{copper}} = 0,0039 \text{ } 1/K$$

Material properties

Specific resistance (ρ)

$$\rho = R \cdot \frac{A}{l} \quad \left[\frac{\Omega \cdot mm^2}{m} \right] = 10^{-6} \Omega \cdot m$$

$$\rho_{\text{copper}} = 0,01786 \frac{\Omega \cdot mm^2}{m}$$

Conductance (G)

G is the reciprocal of R:

$$G = \frac{I}{U} = \frac{1}{R} \quad [S \text{ (Siemens)}]$$

Specific conductivity (γ)

$$\rho = \frac{1}{\gamma} \Rightarrow \gamma = G \cdot \frac{l}{A} \quad \left[\frac{S \cdot m}{mm^2} \right] = 10^6 \frac{S}{m}$$

$$\gamma_{\text{copper}} = 56 \frac{S \cdot m}{mm^2}$$

Resistors in series connection

$$I = I_{\text{TOT}} = I_{R1} = I_{R2} = I_{Rn}$$

$$R_{\text{eq}} = \frac{U_{\text{TOT}}}{I} = \frac{U_{R1} + \dots + U_{Rn}}{I} = R_1 + \dots + R_n$$

Resistors in parallel connection

$$U = U_{R1} = U_{R2} = U_{Rn}$$

$$R_{\text{eq}} = \frac{U}{I_{\text{TOT}}} = \frac{U}{I_{R1} + \dots + I_{Rn}} = \frac{1}{\frac{1}{R_1} + \dots + \frac{1}{R_n}}$$

$$G_{\text{eq}} = \frac{1}{R_{\text{eq}}} = \frac{1}{R_1} + \dots + \frac{1}{R_n}$$

Parallel connection of Two resistors

$$R_{\text{eq}} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{R_1 \cdot R_2}{R_1 + R_2}$$

Linear voltage sources & superposition

Resistance particular cases

- $R = 0 \Omega \rightarrow$ no resistance, perfect wire
- $R = \infty \Omega \rightarrow$ no connection

Linear voltage source

Open circuit

$$R_a = \infty \Rightarrow I = 0; U = U_q$$

Short circuit

$$R_a = 0 \Rightarrow I = I_k = \frac{U_q}{R_i}; U = 0$$

$$\hookrightarrow R_i = \frac{U_q}{I_k} = \frac{\text{source voltage}}{\text{short circ. current}}$$

Normal operating conditions


$$0 < R_a < \infty$$

$$\hookrightarrow U = U_q - U_i = U_q - I \cdot R_i = I \cdot R_a$$


$$\hookrightarrow R_i = \frac{-\Delta U}{\Delta I} = \frac{\text{change of terminal voltage}}{\text{change of load current}}$$

Superposition procedure

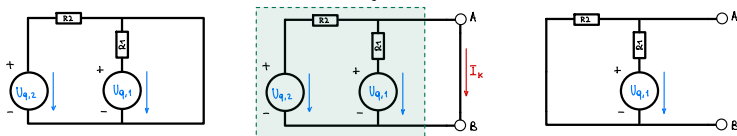1. Select one source and switch off all others ($U = U_q, I = I_k$);
2. Calculate all voltages and currents caused by the chosen single source;
3. Repeat 1. and 2. for each source;
4. Add the contributions of all voltages (Attention to the direction & signs!).



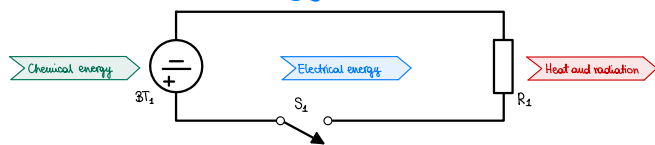Conservation of energy in an electrical circuit



Efficiency (η)

$$\eta = \frac{P_{IN}}{P_{OUT}} \leq 1$$

Conversion of power to mechanical power

$$P_{el} = U \cdot I \rightarrow \text{Motor} \rightarrow P_{mech} = U \cdot I \cdot \eta = M \cdot \omega$$

$$P_{loss} = U \cdot I \cdot (1 - \eta)$$

Conversion of electrical energy to heat energy

$$W_{el} = P_{el} \cdot t = \frac{m \cdot c \cdot \Delta \vartheta}{\eta}$$

Energy costs

$$\text{costs} = W \cdot k, \quad k = \text{energy tariff (0,20 CHF/kWh)}$$

Fields, storage & capacitor + capacitance

Coulumb's law

It calculates the amount of force between two electrically charged particles

$$F = \frac{1}{4\pi\epsilon_0} \cdot \frac{q_1 \cdot q_2}{r^2}; \quad \epsilon_0 = 8,854 \cdot 10^{-12} \frac{\text{As}}{\text{Vm}}$$

Electric field and force on a charge Q

Homogeneous el. fields: $E = \frac{U}{d}$
 E = el. field strength [V/m]
 d = distance of the electrodes [m]

Force on a point charge: $F = Q \cdot E$
 F = force [N]
 Q = charge [As]

Capacitance of a plate capacitor

$$C = \epsilon \cdot \frac{A}{d} \quad [F = \text{Farad}]$$

Permittivity

$\epsilon = \epsilon_0 \cdot \epsilon_r$
 ϵ_0 = absolute permittivity ($8,854 \cdot 10^{-12} \text{ As/Vm}$)
 ϵ_r = relative permittivity of the dielectric, relative to the air

Energy in a capacitor

$$\int_0^{t_{\text{empty}}} U(t) \cdot I dt = \frac{1}{2} U_0 \cdot I \cdot t_{\text{empty}} = \frac{1}{2} C \cdot U_0^2$$

$$\hookrightarrow U(t) = U_0 \left(1 - \frac{t}{t_{\text{empty}}}\right)$$

Capacitors in parallel connection

$$C_{\text{equi}} = \frac{\sum_n Q_n}{U} = \frac{\epsilon \cdot (\sum_n A_n)}{d} = \sum_n C_n = C_1 + C_2 + C_3$$

Capacitors in series connection

$$\frac{1}{C_{\text{equi}}} = \sum_n \frac{1}{C_n} = \frac{Q}{\sum_n U_n} = \frac{\epsilon \cdot A}{\sum_n d_n}$$

Ideal capacitor - voltage relationship

$$i = C \cdot \frac{\Delta U}{\Delta t} \quad \rightarrow \quad \text{Voltage CANNOT instantly jump from one value to another in a capacitor}$$



CR series circuit

$$\begin{cases} U = U_R + U_C \\ i_R = i_C \end{cases}$$

Transient analysis in RC circuits

CR time constant

$$\tau = R \cdot C$$

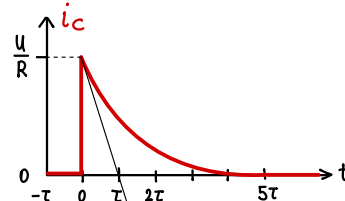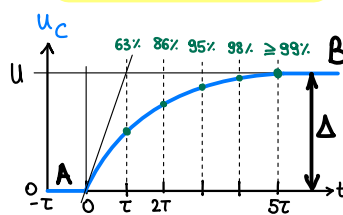

Capacitor charging

$$U_C(t) = U_0 (1 - e^{-t/\tau})$$

$$I_C(t) = \frac{U_0}{R} e^{-t/\tau}$$


Capacitor discharging

$$U_C(t) = U_0 \cdot e^{-t/\tau}$$

$$I_C(t) = -\frac{U_0}{R} e^{-t/\tau}$$


Transitional phase ($0 < t < 5\tau$)
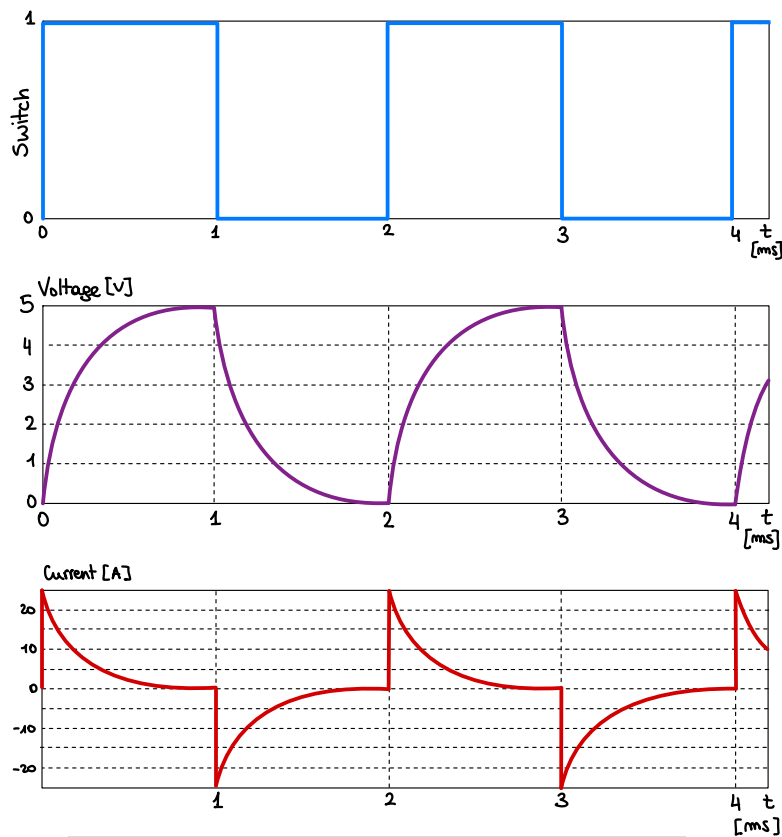
$$f(t) = A + \Delta (1 - e^{-t/\tau}) = A + (B - A)(1 - e^{-t/\tau})$$



Fields, storage & inductor + inductance

Magnetic field H

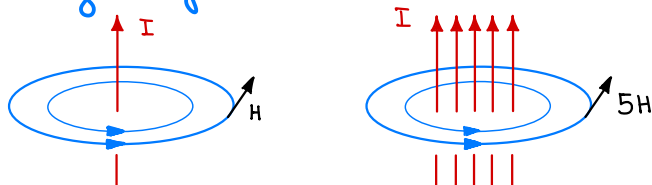

Magnetomotive force (current density)

$$\Theta = N \cdot I \quad ; \quad N = \text{number of turns}$$

Ampère's circuital law

$$\Theta = \oint \vec{H}(\vec{s}) \cdot d\vec{s} = N \cdot I = H \cdot l$$

Magnetic flux density

$$B = \frac{\Phi}{A} = \mu \cdot H = \mu_0 \mu_r \cdot H$$

$$\left[\frac{Vs}{m^2} = T = \frac{Wb}{m^2} = \frac{H}{m} \cdot \frac{A}{m} = \frac{4\pi \cdot 10^{-7} Vs}{m} \cdot [-] \cdot \frac{A}{m} \right]$$


$$\Phi = \sum B\text{-lines} = \text{magnetic flux} \quad \mu_0 = \text{magnetic constant} = 4\pi \cdot 10^{-7}$$

$$\mu = \text{magnetic permeability} \quad \mu_r = \text{relative permeability}$$

$$H = \text{magnetic field strength}$$

Magnetic flux Φ

$$\Phi = B \cdot A$$

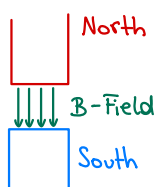


Different μ_r


Material	μ_r
Air	1
Pure iron	$\leq 250'000$
Electrical steel	500...7000
Steel	40...7000
Water	0.999991

Coils with and without iron core

Air core:

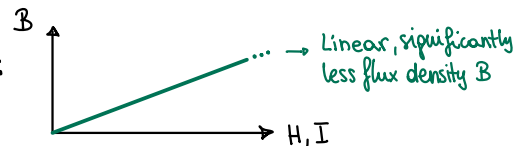

Iron core:

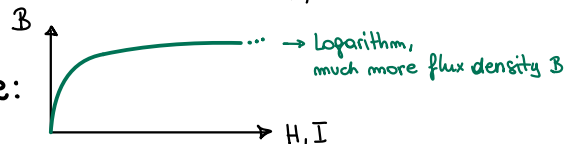

Law of induction and inductance

$$U = -N \cdot \frac{d\Phi}{dt}$$

Stationary case: $\frac{\Delta i}{\Delta t} = 0 \Rightarrow u = 0V$

Inductance and inductor

Inductance (L) is the capability to generate magnetic fields

$$L = \frac{N \cdot \Phi}{I} = U \cdot \frac{\Delta t}{\Delta I} \quad [H \text{ (Henry)} = \frac{[-] \cdot Wb}{A} = \frac{Vs}{A}]$$


Energy in the magnetic field

$$W = \frac{1}{2} L I^2 \rightarrow \text{The current in a coil cannot change abruptly}$$

Current-voltage relationship of an ideal coil

$$u = L \cdot \frac{\Delta i}{\Delta t} \rightarrow \text{Special case: } 0 = \frac{\Delta i}{\Delta t} \rightarrow u = 0$$

Transient analysis in RL circuits

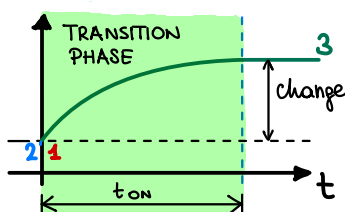



- 1: Starting value $y(0+)$
- 2: State before switching $y(0-)$
- 3: Final value $y(\infty)$

$$\text{Constant } \tau: \tau = L \cdot R_{\text{TOT}}^{-1}$$


Steps:

- 1) $y(0-) = i_L(0-) = i_L(-0)$ since it cannot jump!
- 2) $y(0+) = i_L(0) = i_L(+0)$
- 3) $y(\infty) = i_L(\infty) = i_L(5\tau)$
- 4) $y(t) = i_L(t) = i(\infty) + (i_L(0+) - i_L(\infty))e^{-t/\tau}$

Charging an inductor in a RL-network

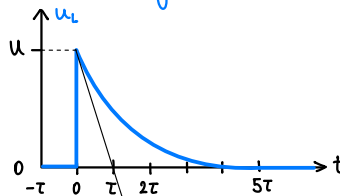
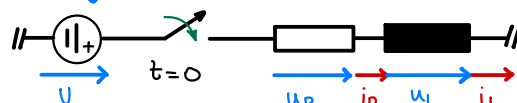

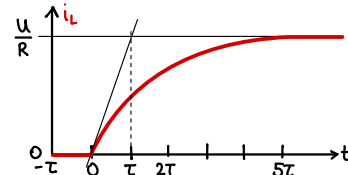
$$u_L = U \cdot \exp\left(-\frac{t}{\tau}\right)$$




$$i_L = \frac{U}{R} \left(1 - \exp\left(-\frac{t}{\tau}\right)\right)$$

Discharging an inductor in a RL-network

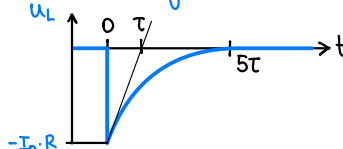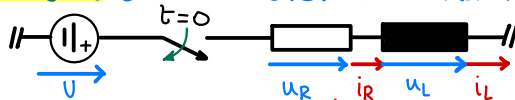

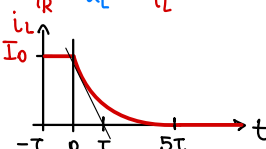
$$u_L = -I_0 R \cdot \exp\left(-\frac{t}{\tau}\right)$$



$$i_L = I_0 \exp\left(-\frac{t}{\tau}\right)$$

Repetition

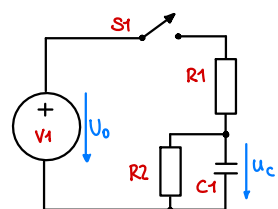

$$u_c(0) = 0$$

$$u_c(\infty) = U_0 \frac{R_2}{R_1 + R_2} = \Delta u_c$$

$$\tau = C(R_1 \parallel R_2)$$


$$u_c(t) = u_c(\infty)(1 - \exp(-t/\tau))$$

$$i_L(0) = 0$$

$$i_L(\infty) = \frac{U_0}{R_1} = \Delta i_L$$

$$i_L(t) = i_L(\infty) \cdot (1 - \exp(-t/\tau))$$

$$\tau = \frac{L}{R_1 \parallel R_2}$$

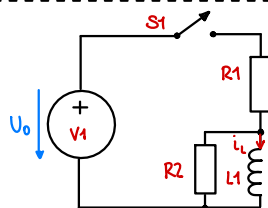

Sinusoidal, effective value, phasors

Voltage oscillation as a function of the angle

$$u(t) = \hat{U} \sin(\omega t)$$

Zero phase angle φ and phase shift

$$u(t) = \hat{U} \sin(\omega t + \varphi_u)$$

$$i(t) = \hat{I} \sin(\omega t + \varphi_i)$$

$$\Delta \varphi = \varphi_u - \varphi_i$$

Power in sin signal and effective value

$$p(t) = u(t) \cdot i(t) = \frac{u(t)^2}{R} = i(t)^2 \cdot R$$

Active power

$$P(t) = \frac{1}{T} \int_0^T p(t) dt$$

Effective value

$$U_{\text{eff}} = \sqrt{\frac{1}{T} \int_0^T u(t)^2 dt} = \frac{\hat{U}}{\sqrt{2}} = \hat{U} \cdot 2^{-1/2}$$

$$I_{\text{eff}} = \dots = \frac{\hat{I}}{\sqrt{2}}$$

Inductive and capacitive reactance

Relationship between current and voltage

on a capacitor: $i = C \cdot \frac{\Delta u}{\Delta t}$

on an ideal inductor: $u = L \cdot \frac{\Delta i}{\Delta t}$

Current waveform

through a capacitor:

Voltage is behind (lags) the current by 90°


through an inductor:

Voltage leads the current by 90°

Reactance


Capacitive
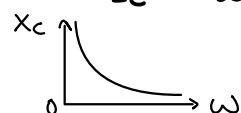
$$X_C = \frac{U_C}{I_C} = \frac{1 \angle -90^\circ}{\omega \cdot C}$$



Reactive
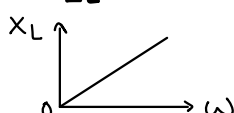
$$X_L = \frac{U_L}{I_L} = \omega L \angle 90^\circ$$




Impedance and admittance

Impedance

$$\underline{Z} \angle (\varphi_u - \varphi_i) = \frac{u(t) \angle \varphi_u}{i(t) \angle \varphi_i}$$

Type of impedance

pure inductive

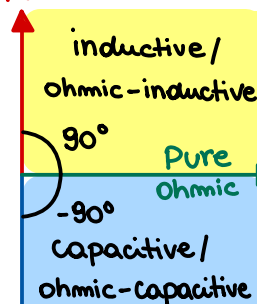

Circuit type	$Z =$	φ_z	P	Q
purely resistive	R	0°	>0	0
purely inductive	$X_L \angle \varphi_L$	$+90^\circ$	0	>0
purely capacitive	$X_C \angle \varphi_C$	-90°	0	<0
resistive - inductive	$R + X_L \angle \varphi_L$	$0^\circ < \varphi_z < +90^\circ$	>0	>0
resistive - capacitive	$R + X_C \angle \varphi_C$	$-90^\circ < \varphi_z < 0^\circ$	>0	<0

pure capacitive

Phase shifts

capacitance

$$\varphi = \tan^{-1}\left(\frac{-X_C}{R}\right)$$

reactivity

$$\varphi = \tan^{-1}\left(\frac{X_L}{R}\right)$$

Series connection

Resistances

$$R_{\text{eq}} = \frac{\sum_i U_{Ri}}{I} = \sum_i R_i$$

Impedances

$$Z_{\text{eq}} = \frac{\sum U_R + \sum U_C \angle \varphi_C + \sum U_L \angle \varphi_L}{I \angle 0^\circ} = \sum_i Z_i$$

Parallel connection

Resistance

$$R_{\text{eq}} = \frac{U}{I} = \frac{U}{\sum_i I_{Ri}} = \frac{1}{\sum_i \frac{1}{R_i}}$$

Impedances

$$Z_{\text{eq}} = \frac{U}{I} = \frac{U}{I \angle 0^\circ} = \frac{1}{\sum_i \frac{1}{Z_i}}$$

Voltage and current phasor


$$\underline{U} = \underline{Z}_{\text{element}} \cdot \underline{I}$$

Power in AC, power factor

Power in electrical circuits

Passive devices (loads)


$$P = U \cdot I > 0$$

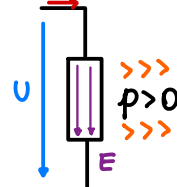

Electrical energy
↓
other form (eg. heat)


Active devices (power sources)

$$P = U \cdot I < 0$$

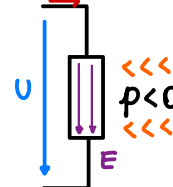


other energy
↓
Electrical energy + power network supply

Conservation of energy

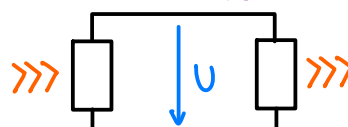

Circuit	Current/ Voltage	Power	Impedance (Admittance)	Signal sequence

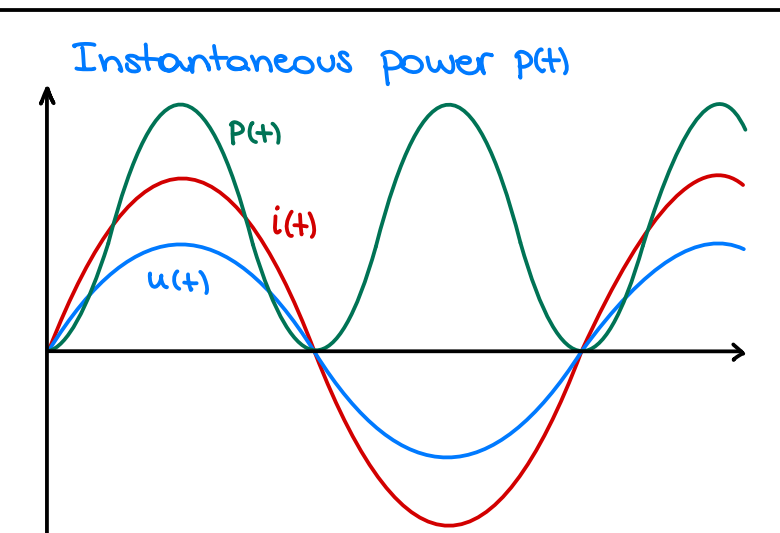

Real power on R

if $\varphi = 0^\circ$

$$P = U \cdot I$$

if $\varphi = \pm 90^\circ$

$$P = 0$$

AC Powers

Apparent power [VA]

$$S = U \cdot I$$

$$S = \sqrt{P^2 + Q^2}$$

Average power [W]

$$P = U \cdot I \cdot \cos \varphi$$

$$P = S \cdot \cos \varphi$$

Reactive power [var]

$$Q = U \cdot I \cdot \sin \varphi$$


$$Q = S \cdot \sin \varphi$$

Power factor

$$\cos \varphi = \frac{P}{S}$$

Performance factor

$$\lambda = \left| \frac{P}{S} \right| = |\cos \varphi|$$

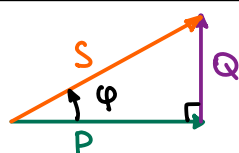

Impedance Z	Real power P	Reactive power Q	Apparent power S
Pure Ohmic $Z = R \angle 0^\circ$ 	$P_R = U_R \cdot I_R = \frac{U_R^2}{R} = I_R^2 \cdot R$	$Q_R = 0 \text{ var}$	$S_R = P$
Pure Capacitive $Z = X_C \angle -90^\circ$ 	$P_C = 0 \text{ W}$	$Q_C = -U_C \cdot I_C = -I_C^2 \cdot X_C = -\frac{U_C^2}{X_C}$ Negative!	$S_C = Q_C $
Pure inductive $Z = X_L \angle +90^\circ$ 	$P_L = 0 \text{ W}$	$Q_L = U_L \cdot I_L = I_L^2 \cdot X_L = \frac{U_L^2}{X_L}$	$S_L = Q_L $
Arbitrary impedance $Z = Z \angle \varphi_Z$ 	$P_Z = U_Z \cdot I_Z \cdot \cos(\varphi_Z)$	$Q_Z = U_Z \cdot I_Z \cdot \sin(\varphi_Z)$	$S_Z = U_Z \cdot I_Z$

Work and Energy

Real energy

$$W_W = P \cdot t$$

Reactive en.


$$W_B = Q \cdot t$$

AC generator

$$U = -N \cdot \frac{\Delta \Phi}{\Delta t}$$

Three-phase circuits

Power transport

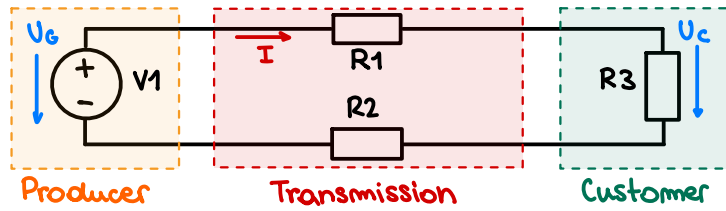


$$P_{\text{PRO}} = U_G \cdot I \quad P_{\text{TRANS}} = (R_1 + R_2) \cdot I^2 \quad P_{\text{CUS}} = U_C \cdot I$$

$$\eta = \frac{P_{\text{CUS}}}{P_{\text{PRO}}} = \frac{P_{\text{PRO}} - P_{\text{TRANS}}}{P_{\text{PRO}}} = 1 - \frac{P_{\text{TRANS}}}{P_{\text{PRO}}}$$


The loss in the line decreases with the square of the U_{TRANS}

Generator

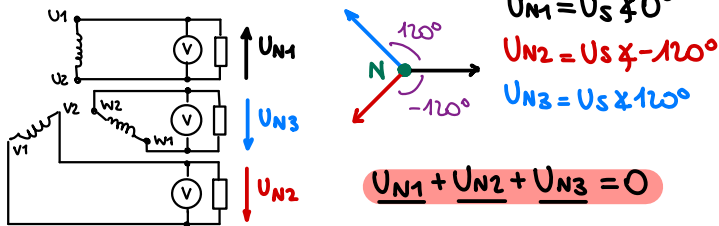

Wye connection


3 connections instead of 6

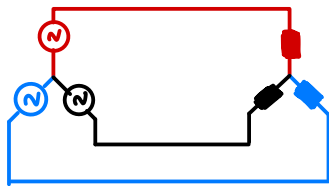

Line voltage → The 3ph sys provides 2 voltages

Phase voltage
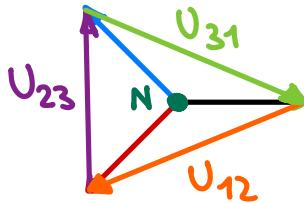
$$\begin{aligned} U_{N1} &= U_s \cdot \sin(\omega t + 0^\circ) \\ U_{N2} &= U_s \cdot \sin(\omega t - 120^\circ) \\ U_{N3} &= U_s \cdot \sin(\omega t + 120^\circ) \end{aligned}$$




Line voltage


$$\begin{aligned} U_{12} &= U_{N2} - U_{N1} = \sqrt{3} U_s \cdot \sin(\omega t - 150^\circ) \\ U_{23} &= U_{N3} - U_{N2} = \sqrt{3} U_s \cdot \sin(\omega t + 90^\circ) \\ U_{31} &= U_{N1} - U_{N3} = \sqrt{3} U_s \cdot \sin(\omega t - 30^\circ) \end{aligned}$$

Wye (Y) and delta (Δ) circuits


Y-config

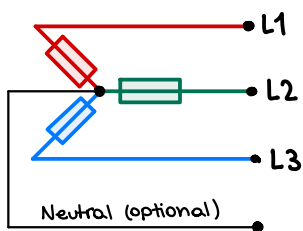

Δ-config

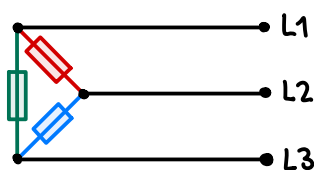


Y-circuit

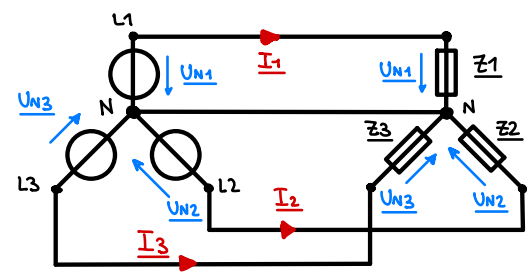

- $Z_1 = Z_2 = Z_3$
- $I = I_s$
- $|I_1| = |I_2| = |I_3|$
- $U = \sqrt{3} U_s$

$$\begin{aligned} S_1 &= U_{N1} \cdot I_1 \\ S_2 &= U_{N2} \cdot I_2 \\ S_3 &= U_{N3} \cdot I_3 \\ S_{\text{TOT}} &= 3 \cdot U_s \cdot I \\ &= \sqrt{3} U I \end{aligned}$$

Δ-circuit

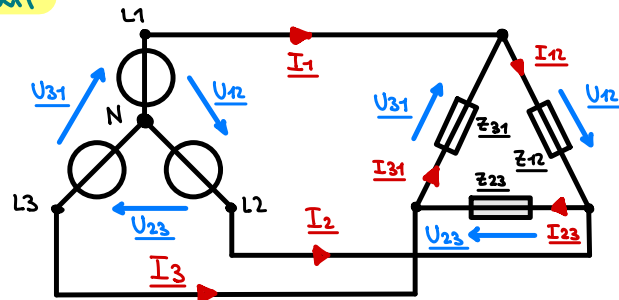

- $Z_{12} = Z_{23} = Z_{31}$
- $I = \sqrt{3} I_s$
- $|I_{12}| = |I_{23}| = |I_{31}|$
- $I_s = \frac{I_1}{\sqrt{3}} = \frac{I_2}{\sqrt{3}} = \frac{I_3}{\sqrt{3}}$
- $U = \sqrt{3} U_s$

$$\begin{aligned} S_{12} &= U_{12} \cdot I_{12} = \sqrt{3} U_{N1} \cdot \frac{I_1}{\sqrt{3}} \\ S_{23} &= U_{23} \cdot I_{23} = \sqrt{3} U_{N2} \cdot \frac{I_2}{\sqrt{3}} \\ S_{31} &= U_{31} \cdot I_{31} = \sqrt{3} U_{N3} \cdot \frac{I_3}{\sqrt{3}} \\ S_{\text{TOT}} &= 3 \cdot U_s \cdot I = \sqrt{3} \cdot U \cdot I \end{aligned}$$

Power calculation

Apparent power [VA] Average power [W]

$$S = 3 \cdot U_s \cdot I = \sqrt{3} \cdot U \cdot I$$

$$P = S \cdot \cos \varphi$$

Reactive power [var]

$$Q = S \cdot \sin \varphi$$

Average power of resistive loads [W]

$$\begin{aligned} P_Y &= 3 \cdot \frac{U_s^2}{R} = \frac{(\sqrt{3} U_s)^2}{R} = \frac{U^2}{R} \\ P_\Delta &= 3 \cdot \frac{(\sqrt{3} U_s)^2}{R} = 3 \frac{U^2}{R} \end{aligned} \quad \left. \vphantom{\begin{aligned} P_Y &= 3 \cdot \frac{U_s^2}{R} \\ P_\Delta &= 3 \cdot \frac{(\sqrt{3} U_s)^2}{R} \end{aligned}} \right\} P_Y = P_\Delta$$